
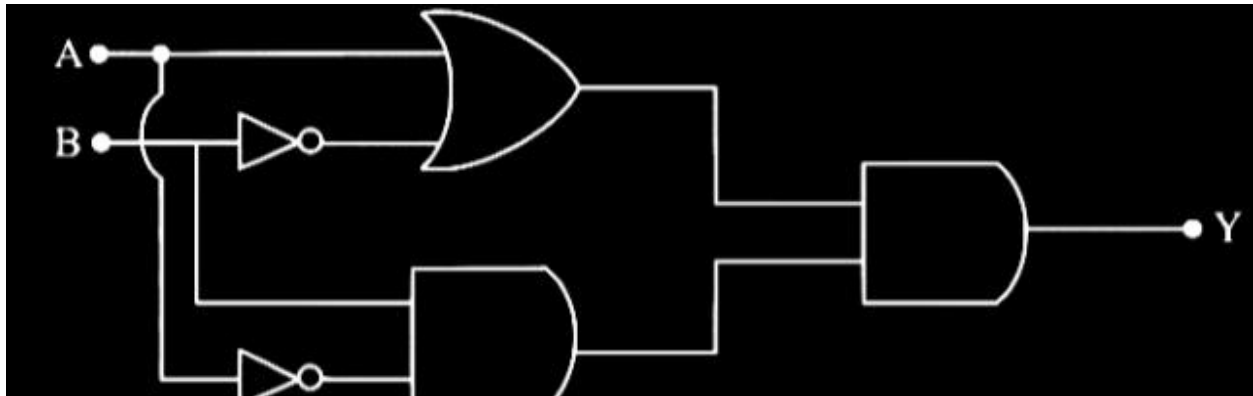


Most Repeated Questions in JEE Main Physics from Logic Gates

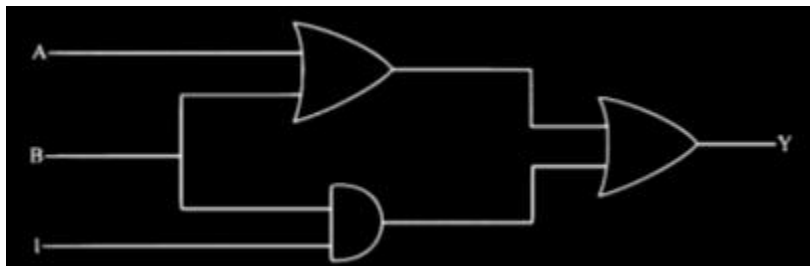Q: The output Y of following circuit for given inputs is :



Q: The output (Y) of logic circuit given below is 0 only when :



Q: Following gates section is connected in a complete suitable circuit.

